TinyWhisper: An Open-Source Fully-Integrated Multi-Mode Short-Wave Transmitter for Amateur Radio Applications in 130-nm CMOS

Simon Dorrer (OE3SDE) Jonathan Hager (DK7JH)
Matthias Jung (DL9MJ) Harald Pretl

2026-11-11

Table of contents

1 Overview **2**
1.1 Purpose . . . 3
1.2 Weak Signal Propagation Reporter . . . 3
1.3 Digital Core . . . 3
1.4 Analog Front-End . . . 4
1.5 Tapeout . . . 4
1.6 Packaging . . . 4
1.7 Outlook . . . 5

2 System Description **5**
2.1 MODEM . . . 5
2.1.1 Coding of Callsign . . . 6
2.1.2 Coding of Locator . . . 7
2.1.3 Coding of Power Level . . . 7
2.1.4 Formation of Data Packet . . . 7
2.1.5 Convolutional Encoding . . . 7
2.1.6 Interleaving . . . 7
2.1.7 Sync Vector and Symbol Formation . . . 8
2.1.8 Data Interface after Modulation . . . 8
2.2 PHY . . . 8
2.2.1 Modulation . . . 9
2.2.2 RF . . . 9

3 Implementation **9**
3.1 Concept . . . 9
3.2 Mixed-Signal Transmitter . . . 10
3.2.1 TX LO Generation . . . 10
3.2.2 TX DACs . . . 11
3.2.3 Lowpass Filters . . . 12
3.2.4 IQ Modulator . . . 12
3.3 Modem . . . 12
3.3.1 CORDIC . . . 12
3.4 Host Interface . . . 13

4 PCB Design **13**

5 Measurements **14**

6 Acknowledgements **14**

> **Warning**
>
> This documentation is a Work in Progress.

> **Important**
>
> This repository requires the IIC-OSIC-TOOLS container with tag `2026.09` or later.

1 Overview

TinyWhisper is a compact WSPR transmitter realized with the ihp-sg13g2 PDK. The 2 mm x 2 mm chip operates at a core supply voltage of 1.5 V and an I/O supply voltage of 3.3 V. The chip is packaged in a QFN-48 package with a total of 56 pins, eight of which are VSS pins connected directly to the package VSS. All documentation, presentations, design files, and future updates are publicly available here. The block diagram is shown below. A render of the final chip layout is shown below, with the digital part placed on the left side of the chip and the analog part on the right. A custom logo on the topmost metal layer, generated with the tool ArtistIC, is also shown below.

Block diagram of the TinyWhisper ASIC and external RF circuitry.

1.1 Purpose

TinyWhisper demonstrates what is possible with current open-source tools and open-source PDKs, from system design to final tapeout, from packaging to PCB design, and even to a 3D-printable enclosure. It can also be used for:

- Ham radio courses
- University courses
- Regression tests of open-source EDA tools

1.2 Weak Signal Propagation Reporter

WSPR is a popular digital transmission scheme in amateur radio, specifically designed to study propagation conditions at low transmit power. WSPR transmits a short message containing the callsign, location, and transmit power using 4-FSK modulation (tone spacing 1.46 Hz, symbol duration 0.683 s). Thanks to strong forward error correction (rate 1/2), long ranges can be achieved even at very low transmit power levels (down to 10 mW). Receivers can decode WSPR signals down to -31 dB below the noise floor of a 2500 Hz channel. Received signals are reported to a central database via the internet, enabling global analysis of signal propagation.

1.3 Digital Core

The heart of the digital core is a simple multi-cycle embedded processor based on a 32-bit RISC-V architecture running at a clock rate of 56 MHz. By using the RISC-V architecture, the CPU is directly compatible with common compilers, and programs can, for example, be written in C. The program is stored in an external SPI SRAM, from which the CPU fetches its instructions. For communication with peripherals, the chip features I2C and UART interfaces as well as digital GPIO pins that can be freely controlled.

An integrated 30-bit CORDIC algorithm generates the 4-FSK-modulated I/Q baseband signals according to the WSPR protocol. The phase increment of the CORDIC can be configured via software, allowing any frequency to be generated with a resolution of approximately 0.05 Hz. This also enables compensation for frequency errors of the external crystal oscillator. Using a second-order Delta-Sigma (DS) modulator with selectable oversampling (32, 64, 128, or 256), the parallel 30-bit data from the CORDIC is converted into a 1-bit signal that is passed directly to the analog front-end. Additionally, the digital core generates the LO frequencies listed in the table below by dividing the 56 MHz clock by two, covering the most common shortwave bands: 28 MHz, 14 MHz, 7 MHz, and 3.5 MHz.

Band	RF Frequency	LO Frequency	IF (CORDIC)
80m	3.568600 MHz	3.5 MHz	68.600 kHz

Band	RF Frequency	LO Frequency	IF (CORDIC)
40m	7.038600 MHz	7 MHz	38.600 kHz
20m	14.095600 MHz	14 MHz	95.600 kHz
10m	28.124600 MHz	28 MHz	124.600 kHz

1.4 Analog Front-End

The analog front-end is an IQ modulator consisting of two third-order multiple-feedback (MFB) low-pass filters with a cutoff frequency of 400 kHz and a Butterworth characteristic. The amplifier core of the MFB filter is based on a Barthelemy / Manfredini (B/M) inverter-based OTA. Two passive voltage-mode mixers are driven by a 25% duty-cycle local oscillator and produce a single-ended RF output signal.

Integrated SPDT switches allow switching between the internal CORDIC/DSM signals and external analog inputs, enabling tests with an external function generator, among other uses.

Since the analog front-end is an IQ modulator, it supports not only WSPR but also other modulation schemes such as FT8, SSB, and CW. Hence, the title "TinyWhisper: An Open-Source Fully-Integrated Multi-Mode Short-Wave Transmitter for Amateur Radio Applications in 130-nm CMOS".

1.5 Tapeout

TinyWhisper was taped out in the IHP open-silicon MPW run of March 2026 as `SoC4219`. The die photo below shows a fabricated chip, with the TopMetal2 logo on top of the core. It is followed by renders of the final layout and of the TopMetal2 logo.

Die photo of the ihp-sg13g2 TinyWhisper ASIC (2mm x 2mm), taped out in March 2026.

Chip render of the ihp-sg13g2 TinyWhisper ASIC (2mm x 2mm).

Render of the TopMetal2 TinyWhisper logo, generated with the tool ArtistIC.

1.6 Packaging

The die is packaged in a QFN-48 open-molded plastic package (OmPP). Its 44 signal and supply pads are wired to package leads. The 12 VSS and IOVSS pads are downbonded to the exposed pad, which forms the package ground, and the 4 VSS and IOVSS leads are bonded to the exposed pad as well. Bonding is done with 25 µm gold wire, the longest wire measures 2.75 mm, and the cover is glued on after bonding.

The bonding diagram below is generated fully automatically with `make bondplan` from the final chip GDS and the EUROPRACTICE package library `EP_PACKAGES_08022018.gds`. The flow extracts the die bondpads together with their names, places the die in the package cavity, draws the bondwires, fills in the title block, and checks wire lengths, crossings, spacing and the clearance around the sensitive RF wires. The pinout and all flow settings are kept in a single configuration file, so the diagram never goes out of sync with the chip. Details are documented in the packaging README.

Bonding diagram of the ihp-sg13g2 TinyWhisper ASIC in a QFN-48 package.

1.7 Outlook

Bare dies of the March 2026 tapeout are back from fabrication, see the die photo in the Tapeout section above. The ASIC is just the beginning of a broader open-hardware project. The next step is to design a PCB that includes all necessary external components: switchable bandpass filters for each RF band, an RF amplifier, a crystal oscillator as the clock source, external SRAM, voltage regulators for the various supply voltages, a display, controls, an SMA connector for the antenna, and a USB interface for configuration. The packaged chip will be soldered onto this board and then characterized.

Building on this PCB, a compact, 3D-printable enclosure is planned that accommodates the board together with a small battery and is robust enough for outdoor use during field tests and SOTA activations.

2 System Description

This TinyTapeout chip implements a transmitter for the long-range wireless protocol **WSPR** (weak signal propagation reporter) in the shortwave frequency range (3 MHz to 30 MHz). Transmissions last $162 \cdot 8192/12000 = 110.6\,\text{s}$ and start at even UTC minutes.

2.1 MODEM

The modulation layer, which packs information into the transmit data packet, works as follows[1]:

- A 50-bit payload is encoded with a convolutional code with $K = 32$ and $r = 1/2$
  - Call sign of 6 characters (A-Z, 0-9, SPACE)
    - Shorter call signs are padded with SPACE to result in 6 characters
    - The 3rd character has to be a number, so insert SPACE in front if needed

[1] https://en.wikipedia.org/wiki/WSPR_(amateur_radio_software)

  - Locator coded with 4 characters (A-Z, 0-9) L_1, L_2, L_3, L_4
    * The first pair of characters takes values from A-R and is encoded using the integers 0-17
    * The second pair of characters are taken from 0-9 and are encoded as that respective number
    * Finally, the locator is encoded as the integer $M_1 = (179 - 10 \cdot L_1 - L_3) \cdot 180 + 10 \cdot L_2 + L_4$
  - Transmit power level in dBm (0 to 60)

- Number of symbols $N_{\text{sym}} = (50 + K - 1) \cdot r^{-1} = 162$
- The baud rate is $12000/8192 = 1.4648\,\text{baud}$
- Synchronization is achieved with a 162-bit constant pseudo-random vector
- Interleaving is used

2.1.1 Coding of Callsign

Starting with a 6-character call sign of [A-Z], [0-9], [SPACE], represented as $C_1, C_2, C_3, C_4, C_5, C_6$.

- Shorter call signs are padded with SPACE to result in 6 characters.
- The 3rd character (C_3) has to be a number, so insert SPACE in front if needed.
- The mapping is:
  - [0]-[9] = 0-9
  - [A]-[Z] = 10-35
  - [SPACE] = 36

The calculation of the integer N representing the call sign is:

$$
\begin{aligned}
N_1 &= C_1 \\
N_2 &= 36 \cdot N_1 + C_2 \\
N_3 &= 10 \cdot N_2 + C_3 \\
N_4 &= 27 \cdot N_3 + C_4 - 10 \\
N_5 &= 27 \cdot N_4 + C_5 - 10 \\
N &= 27 \cdot N_5 + C_6 - 10
\end{aligned}
$$

The resulting N is represented as a 28-bit integer used for transmission[2].

[2] http://www.g4jnt.com/Coding/WSPR_Coding_Process.pdf

2.1.2 Coding of Locator

Location is given as a 4-letter string of [A-Z] and [0-9], represented as L_1, L_2, L_3, L_4. The mapping of the locator:

- The first two characters can be [A]-[R] so are coded as 0-17.
- The second two characters are [0]-[9] coded as 0-9.

The integer M_1 is calculated as:

$$M_1 = (179 - 10 \cdot L_1 - L_3) \cdot 180 + 10 \cdot L_2 + L_4$$

This integer M_1 fits into a 15-bit representation[3].

2.1.3 Coding of Power Level

The transmit power level P is coded in dBm with a range of 0 to 60. The final value of M is coded as:

$$M = 128 \cdot M_1 + P + 64$$

M is represented as a 22-bit integer[4].

2.1.4 Formation of Data Packet

The final 50-bit payload is formed by packing N (28 bit) and M (22 bit) into a 50-bit array. These 50 bits are packed into a 7-byte array D[0] to D[6] (D[0] contains the MSB of the callsign; the LSBs of D[6] are set to zero).

2.1.5 Convolutional Encoding

TBD (see http://www.g4jnt.com/Coding/WSPR_Coding_Process.pdf)

2.1.6 Interleaving

TBD (see http://www.g4jnt.com/Coding/WSPR_Coding_Process.pdf)

[3] http://www.g4jnt.com/Coding/WSPR_Coding_Process.pdf
[4] http://www.g4jnt.com/Coding/WSPR_Coding_Process.pdf

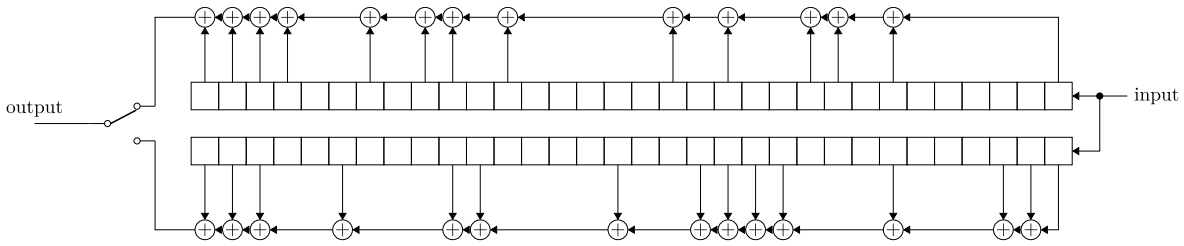


Figure 1: Convolutional Encoder

2.1.7 Sync Vector and Symbol Formation

The resulting 162 bits of data from convolutional coding and interleaving are then combined with a fixed 162-bit synchronization vector.

Each transmission symbol S_i (2 bit for 4-FSK) is formed by ($b_{\text{sync},i}$ is the synchronization bit and $b_{\text{data},i}$ is the data bit)

$$S_i = b_{\text{sync},i} + 2 \cdot b_{\text{data},i}$$

The synchronization vector is given as a 162-bit constant[5]:

```
1100000010001110001001011110000000100101000000101100110100011010000011010101010010010110001101
```

2.1.8 Data Interface after Modulation

The final 162 two-bit symbols are packed as 4 symbols per byte (MSB first) into 41 bytes, resulting in a transmit message M[0] to M[40].

2.2 PHY

WSPR supports various RF frequencies. The frequencies supported by TinyWhisper are[6]:

- 3.568600 MHz (80m band)
- 7.038600 MHz (40m band)
- 14.095600 MHz (20m band)
- 28.124600 MHz (10m band)

[5] http://www.g4jnt.com/Coding/WSPR_Coding_Process.pdf
[6] https://wsjt.sourceforge.io/WSPR_QST_Nov_2010.pdf

These frequencies are the center frequencies (LO frequencies) for the WSPR transmissions. The actual RF output frequency is offset by +1500 Hz using upper-sideband (USB) modulation. For channel selection, the nominal +1500 Hz can be varied in the range of +1400 Hz to +1600 Hz.

2.2.1 Modulation

- 4-FSK with a tone spacing of 1.465 Hz (mode F1D) is used.
- The modulation tone frequencies are:
  - $f_1 = -3/2 \cdot 12000/8192 = -2.197\,\text{Hz}$ (symbol `00`)
  - $f_2 = -1/2 \cdot 12000/8192 = -0.732\,\text{Hz}$ (symbol `01`)
  - $f_3 = 1/2 \cdot 12000/8192 = 0.732\,\text{Hz}$ (symbol `10`)
  - $f_4 = 3/2 \cdot 12000/8192 = 2.197\,\text{Hz}$ (symbol `11`)
- The occupied bandwidth is therefore approximately 6 Hz.
- Minimum SNR for decoding is around $-34\,\text{dB}$.

2.2.2 RF

The RF output of the TinyTapeout chip is a single-ended analog output. It can be used to connect an external power amplifier and low-pass filters to meet the required output power and spectral emissions. Further details can be found in the PCB design section.

3 Implementation

The implementation is targeting a TinyTapeout run using `sky130A` technology, since it allows combining digital and custom components for this WSPR transmitter.

3.1 Concept

The implementation concept is based on a few important boundary conditions listed below:

- A digital clock frequency $f_{\text{clk}} = 56\,\text{MHz}$ is used throughout the design. With this choice of clock frequency the identified transmit frequencies are readily supported.
- For implementation efficiency, the digital content of the architecture is maximized in contrast to the full-custom content.

3.2 Mixed-Signal Transmitter

The architectural overview is shown in Figure 2. The FSK-4 modulation is based on an analog IQ transmitter driven by a CORDIC. An IQ DAC path with a sample rate of 218.75 kSps (TBC) and a CORDIC/DSM data path width of 30 bit, followed by a 3rd-order low-pass filter, is upconverted in a passive voltage-mode mixer with 25% LO generated by a divide-by-2 circuit.

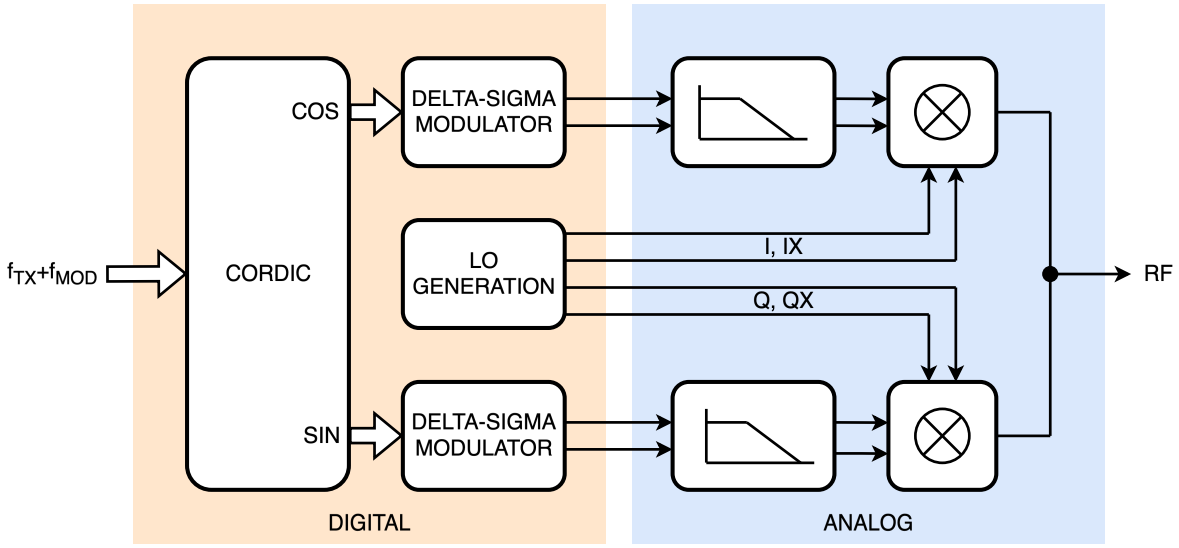


Figure 2: Architecture of the mixed-signal WSPR transmitter.

3.2.1 TX LO Generation

To support the RF frequencies listed in Section 2.2, the following LO generation concept is planned. The LO frequency is 2x the RF frequency, since the IQ phases are generated by a divide-by-2 circuit (https://iic-jku.github.io/radio-frequency-integrated-circuits/rfic.html#sec-lo-ff). If a constant 56 MHz crystal clock is used, the resulting frequency offset must be generated digitally by the CORDIC.

RF frequency	LO frequency	LO pre-divider	CLK frequency	CORDIC frequency offset
3.592600 MHz	7 MHz	8	56 MHz	92.600 kHz
7.038600 MHz	14 MHz	4	56 MHz	38.600 kHz
14.095600 MHz	28 MHz	2	56 MHz	95.600 kHz
28.124600 MHz	56 MHz	1	56 MHz	124.600 kHz

As the frequencies are low enough, the LO generation is implemented in HDL in `src/lo_gen.v`.

3.2.2 TX DACs

To simplify the analog DAC design, delta-sigma DACs (DSM) with differential single-bit outputs are used. As a compromise between implementation complexity and performance, a programmable 1st/2nd-order modulator is used, which can be implemented purely digitally in HDL with inverter-style outputs.

The output sample rate of the DS modulator is 56 MSps, and it supports OSR = 32/64/128/256. The corresponding input sample rates are given in the following table:

OSR	Input sample rate
32	1.75 MSps
64	875 kSps (default)
128	437.5 kSps
256	218.75 kSps

The general SNR formula for an N-bit, L-order DSM with OSR is[7]

$$\mathrm{SNR} = 6.02N + 1.76 + 10\log_{10}\left(\frac{2L+1}{\pi^{2L}}\right) + (2L+1)10\log_{10}(\mathrm{OSR}).$$

The SNR of a single-bit ($N = 1$) first-order ($L = 1$) DSM is given by ($r = \log_2(\mathrm{OSR}) = 6$ for an OSR = 64)

$$\mathrm{SNR} = 6.02 + 9.03r - 3.41 = 56.8\,\mathrm{dB},$$

which motivates using a higher-order DSM for improved in-band SNR. A second-order ($L = 2$) DSM with single-bit ($N = 1$) output is given by

$$\mathrm{SNR} = 6.02 + 15.05r - 11.14 = 85.2\,\mathrm{dB},$$

which provides significantly higher in-band SNR and supports high-resolution signal generation. In the current TinyWhisper architecture, the CORDIC uses a 30-bit data path and the DSM consumes this high-resolution parallel data before 1-bit quantization. The DSM order is selectable (1st or 2nd order), and this option is programmable via a configuration register.

The data width of the input samples is configurable; the current TinyWhisper implementation uses a 30-bit CORDIC/DSM path. The input data is linearly interpolated to the 56 MSps

[7] Norsworthy, Schreier, Temes, "Delta-Sigma Data Converters", Wiley, 1997.

output sample rate. The interpolation is done by a linear ramp between two input samples, with step size depending on the OSR (i.e., for OSR = 64 the step size is $(\text{data}_{n+1} - \text{data}_n)/64$).

The DSM is implemented in `src/dsmod.v`.

3.2.3 Lowpass Filters

To pass the maximum CORDIC frequency offset of around $f_{\text{mod,max}} = 125\,\text{kHz}$ through the filters, we assume a nominal filter $-3\,\text{dB}$ cutoff frequency of $f_c = 400\,\text{kHz}$. This allows the use of untrimmed filters with an assumed RC-product frequency variation of $\pm 30\%$. With a maximum frequency deviation to $f_{c,\text{max}} = 1.3 \cdot f_c = 520\,\text{kHz}$, and assuming a third-order low-pass response, the DAC aliasing at 56 MHz is suppressed by $> 100\,\text{dB}$. A minimum filter corner frequency of $f_{c,\text{min}} = 0.7 \cdot f_c = 280\,\text{kHz}$ still passes the maximum modulation frequency comfortably.

We select a 3rd-order filter based on the argument that the DS-modulator in the DAC is second order; so to suppress the rising quantization noise with a slope of $40\,\text{dB/dec}$ we opt for a 3rd-order filter with a filter slope of $60\,\text{dB/dec}$.

3.2.4 IQ Modulator

The IQ modulator is implemented as a passive voltage-mode mixer. The 4 LO phases generated in the LO generation block drive 4 transmission gates (to switch rail-to-rail voltage signals coming out of the low-pass filters). These transmission gates are directly DC-connected to the 2 differential outputs of the IQ low-pass filters driven by the OTA. Since 25% LO signals are used, there is only minimal overlap between LO phases, so the mixer switch outputs can simply be connected (added).

As the digital LO generation block generates 4 single-ended LO signals, the transmission gates include local drivers including creation of an inverted clock to drive the NMOS and PMOS of the transmission gates. Cross-coupling latches reduce the potential overlap of the LOP/LON phases.

The resulting single-ended RF output is directly connected to an analog output of the Tiny-Tapeout chip to drive external circuitry like lowpass filters and an amplifier.

3.3 Modem

3.3.1 CORDIC

The CORDIC creates the modulation frequencies of the 4-FSK modulation (see Section 2.2.1), and also creates the required frequency offset for transmit frequency generation (see Section 3.2.1). The CORDIC produces a COS/SIN output signal with a sample rate of 875 kSps =

56 MHz/64 (TBC) and a 30-bit word size, matching the high-resolution digital signal path described in Section 3.2.2.

Assuming a TCXO initial frequency error of ±5 ppm (TBC) of the 56 MHz clock, the CORDIC needs to be able to correct an additional ±280 Hz of frequency offset.

As the CORDIC shall only produce a new sample every OSR = 64 clock cycle, a new sample is pulled from the CORDIC by the DSM by asserting its `o_data_rd` output.

3.4 Host Interface

On TinyTapeout, a 16-bit digital input and an 8-bit digital output are available. However, to simplify the programming interface, a one-wire UART protocol is used. The following registers are available:

Addr	Number of bits	Comment
0	d.c.	Reset
1	3	lo_div selection
2	16	f_c0[15:0] (cordic f_c for the first symbol)
3	16	OSR_0 & f_c0[29:16]
4	16	f_c1[15:0]
5	16	OSR_1 & f_c1[29:16]
6	16	f_c2[15:0]
7	16	OSR_2 & f_c2[29:16]
8	16	f_c3[15:0]
9	16	OSR_3 & f_c3[29:16]
10	12	callsign[34:24]
11	12	callsign[23:12]
12	12	callsign[11:0]
13	15	locator[19:5]
14	11	locator[4:0] & power

The Python script in the software directory takes care of programming the registers.

4 PCB Design

Coming soon…

5 Measurements

Coming soon...

6 Acknowledgements

This project is funded by the JKU/SAL IWS Lab, a collaboration of Johannes Kepler University and Silicon Austria Labs.